

Chapter 11: AC Power Analysis

(11.1) Effective or RMS VALUE:

$$X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2 dt}$$

$$X_{\text{rms}} = \frac{X}{\sqrt{2}} \text{ (only valid for sinusoidal functions)}$$

If not a sinusoidal then:

$$X_{\text{rms}} = \sqrt{\frac{1}{T} \left(\int_0^T (x_1^2) dt + \int_0^T (x_2^2) dt + \dots + \int_0^T (x_n^2) dt \right)}$$

The effective value: of a periodic current is the dc current that delivers the same average power to a resistor as the sinusoidal periodic current.

(11.2) COMPLEX POWER

Complex power of an Impedance Z:

$$S = I_{\text{rms}}^2 Z = \frac{V_{\text{rms}}^2}{Z^*} = V_{\text{rms}} I_{\text{rms}}^*$$

Angle of Impedance:

$$\theta_z = \angle(\tilde{Z}) = \angle(\tilde{S})$$

Complex Power (for any Circuit Element):

$$\text{Complex Power} = S = P + jQ = V_{\text{rms}}(I_{\text{rms}})^* \\ = |V_{\text{rms}}| |I_{\text{rms}}| \angle \theta_v - \theta_i$$

$$\text{Apparent Power} = S = |S| = |V_{\text{rms}}| |I_{\text{rms}}| = \sqrt{P^2 + Q^2}$$

$$\text{Real Power} = P = \text{Re}(S) = S \cos(\theta_v - \theta_i)$$

$$\text{Reactive Power} = Q = \text{Im}(S) = S \sin(\theta_v - \theta_i)$$

$$\text{Power Factor} = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

Lagging power factor when $\theta_v - \theta_i > 0$

Leading power factor when $\theta_v - \theta_i < 0$

Reactive factor: $r_f = \sin(\theta_z)$

1. $Q = 0$ for resistive loads (unity pf).
2. $Q < 0$ for capacitive loads (leading pf).
3. $Q > 0$ for inductive loads (lagging pf).

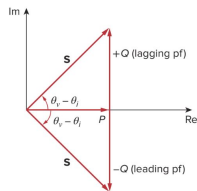


Figure 11.22 Power triangle.

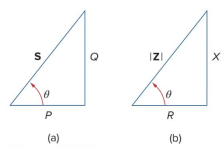


Figure 11.21 (a) Power triangle, (b) impedance triangle.

Conservation Of Complex Power:

(assumed using passive sign conv)

For Series:

$$\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2$$

$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = (\mathbf{V}_1 + \mathbf{V}_2)\mathbf{I}^* = \mathbf{V}_1\mathbf{I}^* + \mathbf{V}_2\mathbf{I}^* = \mathbf{S}_1 + \mathbf{S}_2$$

For parallel:

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2$$

$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = \mathbf{V}(\mathbf{I}_1^* + \mathbf{I}_2^*) = \mathbf{V}\mathbf{I}_1^* + \mathbf{V}\mathbf{I}_2^* = \mathbf{S}_1 + \mathbf{S}_2$$

$$\tilde{S}_1 + \tilde{S}_2 + \dots + \tilde{S}_n = 0$$

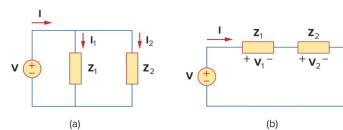


Figure 11.23 An ac voltage source supplied loads connected in: (a) parallel, (b) series.

Maximum Average Power transfer(ALL MAX):

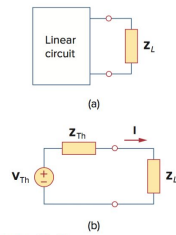


Figure 11.7 Finding the maximum average power transfer: (a) circuit with a load, (b) the Thevenin equivalent.

$$\tilde{Z}_{Th} = R_{Th} + jX_{Th}$$

$$\tilde{Z}_L = R_L + jX_L$$

$$P = \frac{1}{2} |\tilde{I}|^2 R_L = \frac{|\mathbf{V}_{Th}|^2 R_L / 2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

After taking the partial of $P(\tilde{Z}_L)$ with respect to R_L and X_L we get:

$$R_L(X_L) = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2}$$

$$X_L = -X_{Th}$$

If ($\tilde{Z}_L = R_L + jX_L$):

$$P_{max} = P(\tilde{Z}_{Th}^*) = \frac{|\mathbf{V}_{Th}|^2}{8R_{Th}}$$

If else ($\tilde{Z}_L = R_L$):

$$P_{max} = P(|\tilde{Z}_{Th}|) = \frac{1}{2} \frac{|\mathbf{V}_{Th}|^2 |\tilde{Z}_{Th}|}{[|\tilde{Z}_{Th}|^2 + R_{Th}^2 + X_{Th}^2]}$$

Chapter 12: Three - Phase Circuits(RMS Eqns)

Balanced phase Voltages: are equal in magnitude and are out of phase with each other by 120

$$V_{an} + V_{bn} + V_{cn} = 0$$

$$V_{an} = V_{bn} = V_{cn}$$

Phase Sequence: is the time order in which the voltages pass through their respective maximum values.

Positive Sequence(abc):

$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle -120^\circ \\ V_{cn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$

Negative Sequence(acb):

$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{cn} &= V_p \angle -120^\circ \\ V_{bn} &= V_p \angle -240^\circ = V_p \angle +120^\circ \end{aligned}$$

Balanced load: is one in which the phase impedances are equal in magnitude and in phase.

$\Delta - > Y$ Transformations:

$$\tilde{Z}_Y = \frac{1}{3} \tilde{Z}_\Delta$$

$$V_{\phi,Y} = \frac{1}{\sqrt{3}} V_{\phi,\Delta} \quad \text{Line-Phase relationship}$$

Phasor diagrams

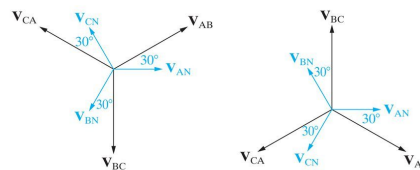


Figure 11.9 Phasor diagrams showing the relationship between line-to-line and line-to-neutral voltages in a balanced system. (a) The abc sequence, (b) The bca sequence.

For negative sequence:

$$\tilde{V}_{AB} = \sqrt{3} \tilde{V}_{AN} \angle -30$$

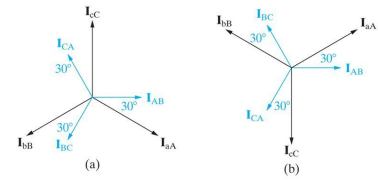


Figure 11.13 Phasor diagrams showing the relationship between line currents and phase currents in a Δ -connected load. (a) The positive sequence, (b) The negative sequence.

Copyright 2013 by Pearson Education, Inc. All rights reserved. PEARSON

For negative sequence:

$$\tilde{I}_{AB} = \sqrt{3} \tilde{I}_{aA} \angle -30$$

EQUATIONS FOR SOLVING 3 - phase

TABLE 12.1

Summary of phase and line voltages/currents for balanced three-phase systems.¹

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ Same as line currents	$V_{ab} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = V_{an} / Z_Y$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y- Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = V_{AB} / Z_\Delta$ $I_{BC} = V_{BC} / Z_\Delta$ $I_{CA} = V_{CA} / Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3} V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ - Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = V_{ab} / Z_A$ $I_{BC} = V_{bc} / Z_B$ $I_{CA} = V_{ca} / Z_C$	Same as phase voltages $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ -Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ Same as line currents	$I_a = \frac{V_p \angle -30^\circ}{\sqrt{3} Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

¹Positive or abc sequence is assumed.

Power in a Balanced Load:

Instantaneous power in a three phase balanced system:

$$P_{3\phi} = 3V_{\phi} I_{\phi} \cos \theta_z$$

This result is true for either y or delta connected load

Per-Phase Powers:

$$P_{\phi} = p/3 = V_{1\phi} I_{\phi} \cos \theta_z$$

$$Q_{\phi} = V_{\phi} I_{\phi} \sin \theta_z$$

$$\tilde{S}_{\phi} = P_{1\phi} + j Q_{1\phi} = \tilde{V}_{1\phi} \tilde{I}_{1\phi}^*$$

The total average power is the sum of the average powers in the phases:

$$P_{3\phi} = P_a + P_b + P_c = 3P_{\phi} = 3V_{\phi} * I_{\phi} \cos \theta_z = \sqrt{3} V_L I_L \cos \theta_z$$

For Y-connected load: $I_L = I_{\phi}$ but $V_L = \sqrt{3} V_{\phi}$

For Δ - connected load: $I_L = \sqrt{3} I_{\phi}$ but $V_L = V_{\phi}$

$$Q_{3\phi} = 3Q_{\phi} = \sqrt{3} V_L * I_L \sin(\theta_{\phi})$$

And then total complex power of a 3 phase system:

$$\tilde{S}_{3\phi} = 3\tilde{S}_{\phi} = 3\tilde{V}_{\phi} \tilde{I}_{\phi}^* = 3I_{\phi}^2 \tilde{Z}_{\phi} = 3 \frac{V_{\phi}^2}{\tilde{Z}_{\phi}^*}$$

OR

$$\tilde{S}_{3\phi} = P_{3\phi} + jQ_{3\phi} = \sqrt{3} V_L I_L \angle \theta_{\phi}$$

Where :

θ_{ϕ} is the phase angle of that element or impedance angle

Don't make the mistake of:

$$S_{3\phi} \neq \tilde{V}_L \tilde{I}_L^* \neq \sqrt{3} V_L I_L \angle \theta_\phi$$

Power Calculation in 3-phase circuits: (TIPS)

See what is given:

1.) Look what you are given

a.) Case 1: given just impedances or Currents/ Voltages:

- Try to change everything to a Y - Y configuration

-> If (there are multiple balanced loads given) {
When (L1 and L2 are in parallel):

Transform L1 and L2 to Y forms and connect combine their individual impedances.

Then Make single phase equivalent circuit.

b.) Case 2: given just the a Power quantity

- Notice that $S_{\phi,Y} = S_{\phi,\Delta}$
- That means we can make a single equivalent directly of individual Loads.

c.) case 3: Combination of case 1 and 2

- Try to break this circuit in a single phase equivalent (convert everything to Y)
- For the Load given a Power quantity with a black box use the fact that $S_{\phi,Y} = S_{\phi,\Delta}$

-> Next the circuit build the single phase circuit

2.) Once you Configured your Circuit. If not given a reference set one:

Example: You might be given a magnitude, and there is not way to even solve for a variable need with this magnitude. Therefore give the phasor a reference angle of 0.

If you are given a line voltage but need to use line to neutral voltage make it such that line to voltage phase is your reference.

3.) Solve using or method :

On Calculator function for parallel impedances:
 $z1(x,y) = x || y$

Source Transformations:

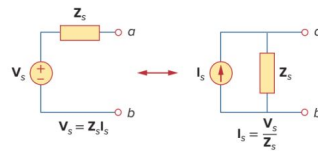


Figure 10.16
Source transformation.

$$V_s = Z_s I_s \Leftrightarrow I_s = \frac{V_s}{Z_s}$$

Three phase - Circuit visuals (assuming Positive sequence):

Y-Y Balanced circuit:

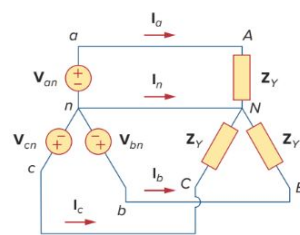


Figure 12.10
Balanced Y-Y connection.

Alternative way of analyzing a balanced Y-Y system:

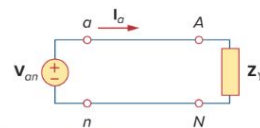


Figure 12.12
A single-phase equivalent circuit.

Balanced Y - Δ :

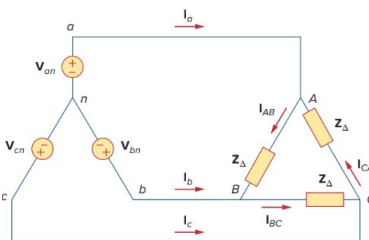


Figure 12.14
Balanced Y-Δ connection.

Alternative way of analyzing a balanced Y-Δ :

Balanced Δ - Y:

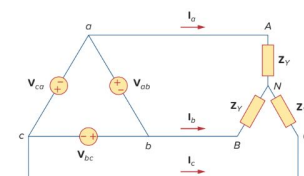


Figure 12.18
A balanced Δ-Y connection.

Alternative way of analyzing Δ - Y balanced:

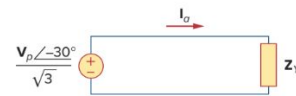


Figure 12.20
The single-phase equivalent circuit.

Balanced Δ - Δ :



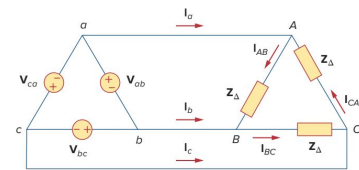


Figure 12.17
A balanced Δ-Δ connection.

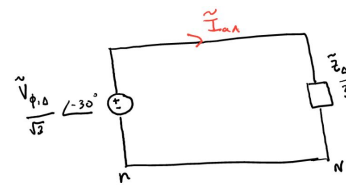Alternative way of analyzing Δ - Y balanced:



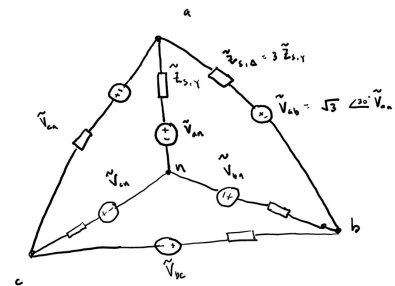A Three phase source with winding impedance:



Help: (POWER LOSS)

What percentage of the average power at the sending end of the line is delivered to the loads?

$$\% \text{ diff} = \frac{P_{s,\phi} - P_{l,\phi}}{P_{s,\phi}} \cdot 100 \%$$

